
CS147 - Lab 16

Gate Level Modeling


Kaushik Patra (kaushik.patra@sjsu.edu)


1


Implement 32-bit 32x1 MUX

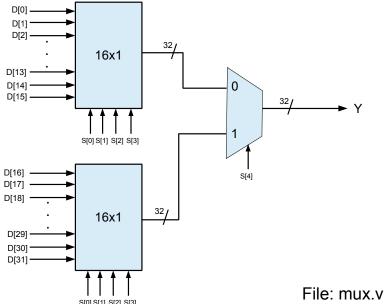


Implement 2-to-4 line decoder The second of the second of

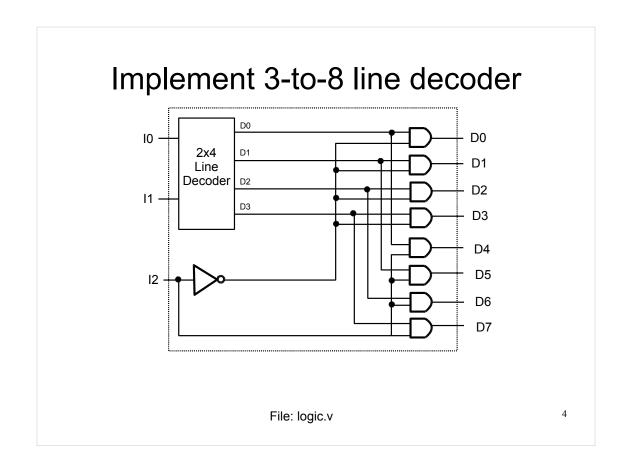

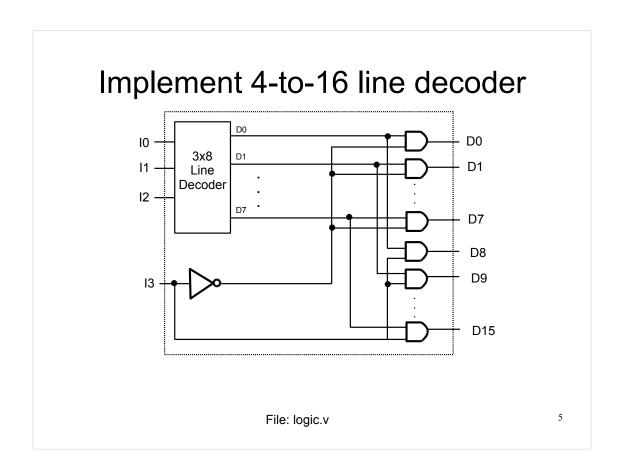

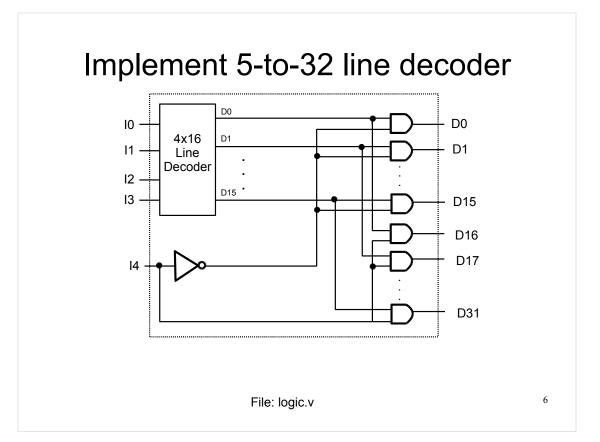

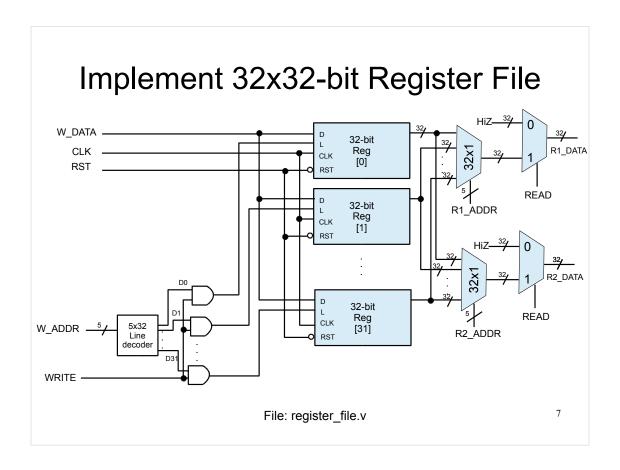

CS147 - Lab 15

Gate Level Modeling

Kaushik Patra (kaushik.patra@sjsu.edu)

8